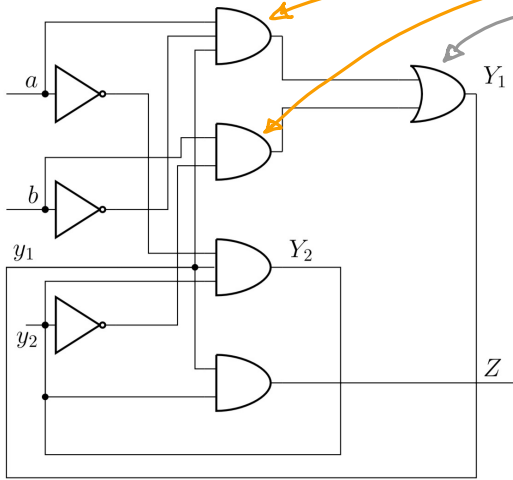


Q1 Logic equations, Muffman Table & state graph

a)



$$Y_1 = \text{OR}(\text{AND}(a, \bar{b}, y_1), \text{AND}(b, \bar{y}_2))$$

$$Y_1 = a\bar{b}y_1 + b\bar{y}_2$$

$$Y_2 = \text{AND}(\bar{a}, y_1, y_2) = \bar{a}y_1y_2$$


$$Z = \text{AND}(y_1, y_2) = y_1y_2$$

Logic equations

Muffman Table


		ab				
y_1	y_2	00	01	11	10	Z
0	0	00	10	10	00	0
0	1	00	00	00	00	0
1	1	01	01	00	10	1
1	0	00	10	10	10	0
y_1	y_2					

Put y_2
Put y_1

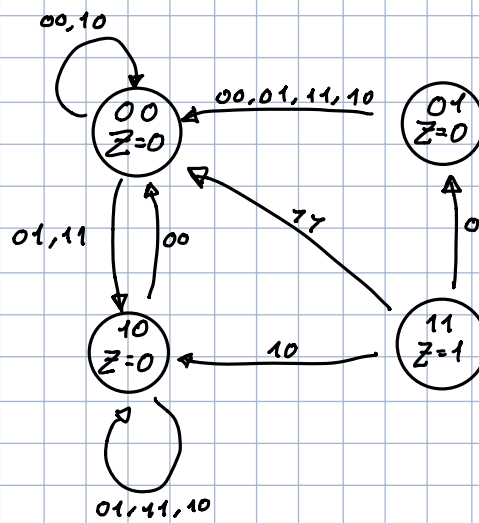

State graph

b)

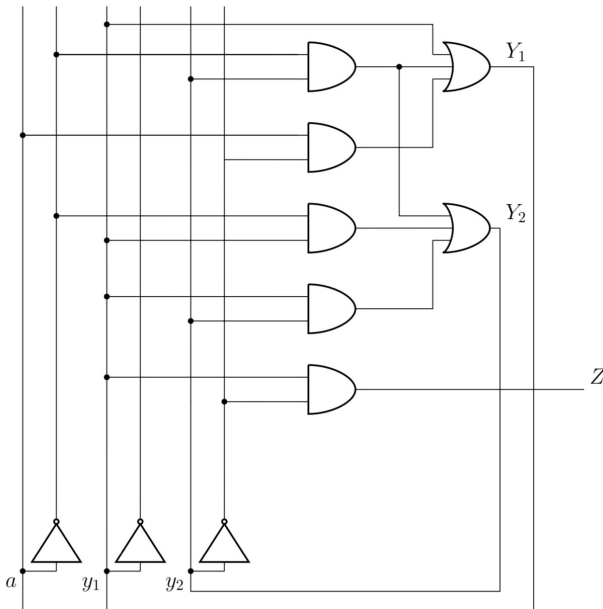

Logic equations

$$Y_1 = + (y_1, \cdot (\bar{a}, y_2), \cdot (a, \bar{y}_2))$$

$$Y_1 = y_1 + \bar{a}y_2 + a\bar{y}_2$$

$$Y_2 = + (\cdot (\bar{a}, y_2), \cdot (\bar{a}, y_1), \cdot (y_1, y_2))$$


$$Y_2 = \bar{a}y_2 + \bar{a}y_1 + y_1y_2$$

$$Z = \cdot (y_1, \bar{y}_2) = y_1\bar{y}_2$$

Muffman Table :

		ab				
y_1	y_2	00	01	11	10	Z
0	0	00	00	10	10	0
0	1	11	11	00	00	0
1	1	11	11	11	11	0
1	0	11	11	10	10	1
y_1	y_2					

State graph

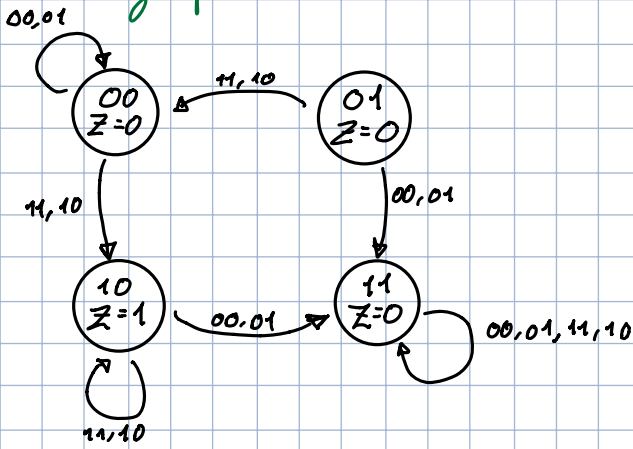

Q3

$$f(a, b, c, d, e) = \sum_m (0, 2, 5, 7, 8, 9, 10, 11, 13, 23, 26, 27, 29) + \sum_d (3, 12, 15, 18, 19, 21, 22, 31)$$

	F	00	01	11	10	de
0	000	1	0	-	1	
1	001	0	1	1	0	
3	011	-	1	-	0	
2	010	1	1	1	1	
4	100	0	0	0	-	
5	101	0	-	1	-	
7	111	0	1	-	0	
6	110	0	0	1	1	



abc

$$F = \bar{a}\bar{b}\bar{c} + \bar{a}ce + ce + \bar{c}d$$

Q2: Question 2. A door opener is controlled by a password that is controlled using two buttons a and b . We assume that the value associated to each button equals 1 when the button is pressed, 0 otherwise. The door is being opened if the output Z_1 is set to 1, which happens whenever the last button of the password is pressed. The code is the following: press and release a two times, then press and release b and finally press and release a again. Any wrong sequence sets the output Z_2 to 1, triggering the alarm. Once activated, the alarm stays active whatever the input. Build the state graph and Huffman table for this problem.

1) Identify states & make a diagram

2) Convert to state graph

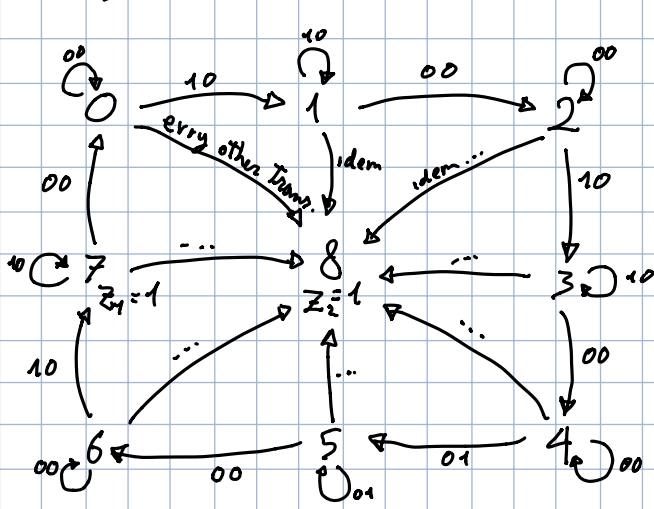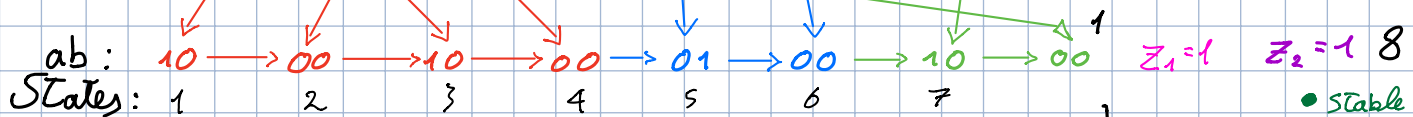

ab

$y_1 y_2 y_3 y_4$	00	01	11	10	Z_1	Z_2
0000	0000	1000	1000	0001	0	0
0001	0010	1000	1000	0001	0	0
0010	0010	1000	1000	0011	0	0
0011	0100	1000	1000	0011	0	0
0100	0100	0101	1000	1000	0	0
0101	0110	0101	1000	1000	0	0
0110	0110	1000	1000	0111	0	0
0111	0000	1000	1000	0111	1	0
1000	1000	1000	1000	1000	0	1

$y_1 y_2 y_3 y_4$

• Stable states
• Alarm state